



TÉCNICO
LISBOA

Circuit Theory and Electronics Fundamentals

Integrated Masters in Aerospace Engineering, Técnico, University of Lisbon

Laboratory Report 4- Group 28

Beatriz Pedroso 95773, Teresa Gonçalves 95826, Tiago Escalda 95851

22th May, 2021

Contents

1 Introduction 3

2 Theoretical Analysis 4

2.1 Gain Stage 4

2.2 Output Stage 4

2.3 Final Results 5

3 Simulation Analysis 7

4 Comparison 10

5 Conclusion 12

1 Introduction

The aim of this laboratory assignment was to create an audio amplifier circuit and analyse the circuit both theoretically and using *Ngspice*. To do so, both the gain and the output stages were designed. This amplifier receives an audio maximum input of 10mV and connects to an 8 Ohm speaker. The source has an impedance of 100 Ohms and the circuit is supplied by a 12V Voltage DC source (vcc).

In the gain stage mentioned above, a NPN transistor and a common emitter amplifier with degeneration were used. It allows us to have a high Z_i and a high A_V . Nevertheless, Z_o is also very high, which constitutes a problem. Hence, this situation has to be addressed in the output stage. Consequently, in this second stage, it was used a common collector amplifier and a PNP transistor. Not only does it allow to remain a high A_V but it also reduces the value of (Z_o) significantly. Therefore, the gain in the common collector amplifier is ≈ 1 , which is the desired result.

The quality of the audio amplifier is evaluated by the following expression:

$$MERIT = \frac{VoltageGain * Bandwidth}{Cost * LowerCutOffFrequency} \quad (1)$$

The circuit is shown below as well as the values associated to each component (in V, Ohm and Farads).

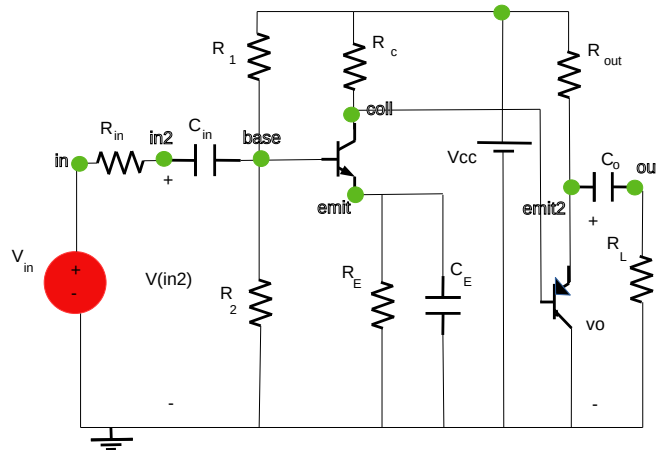


Figure 1: Circuit in analysis.

Name	Value
Cin	5.000000e-04
CE	5.000000e-04
Cout	2.000000e-04
R1	2.000000e+04
R2	2.000000e+03
RC	3.000000e+03
RE	1.000000e+02
Rout	1.000000e+02
Vcc	1.200000e+01

Table 1: Used Values of each component.

2 Theoretical Analysis

In this section, a theoretical analysis of the circuit was conducted. In the introduction, we can see the analysed circuit.

First of all, we got to keep in mind that our circuit is divided in two different stages. The first one corresponds to the gain stage with a NPN transistor and the second is the output stage with a PNP transistor. Both the components and their functions will be described in Theoretical and Simulation Analysis as well as the goal of each stage.

2.1 Gain Stage

This stage is responsible for the signal amplification which means it has to have a high gain. It also needs to have a high input voltage to avoid signal losses. In order to analyse this stage we need to study both operating point and incremental analysis. First, we compute a simple analysis of the circuit by KVL and KCL. This way we obtain $Z_{i1} = R_B || r_{\pi 1}$ and $Z_{o1} = r_{o1} || R_c$. It is important to note that for low frequencies capacitors behave like open circuits and for high frequencies like short circuits.

To analyse the incremental response we have to create a model of the transistor (and the rest of the gain stage) similar to Fig.2. Studying the circuit we get $v_{o1} = -g_m * (r_o || R_c) * v_{\pi}$ and $v_{\pi} = \frac{R_B || r_{\pi 1}}{R_B || r_{\pi 1} + R_s} * v_s$ which lead us to $A_{v1} = \frac{v_{o1}}{v_s} = -g_m * (r_o || R_c) * \frac{R_B || r_{\pi 1}}{R_B || r_{\pi 1} + R_s}$.

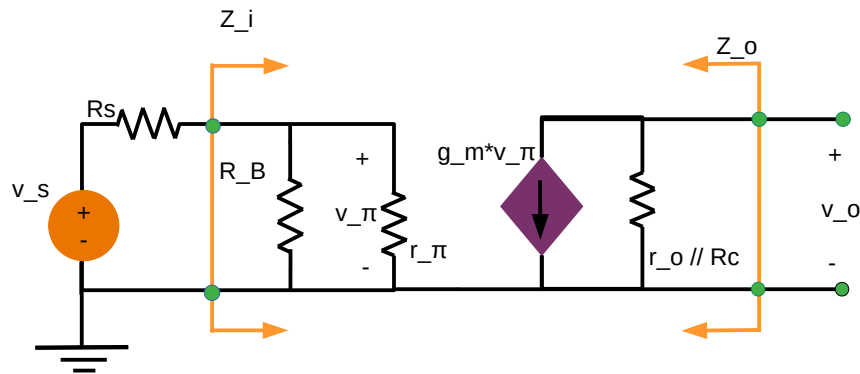


Figure 2: Model for the gain stage incremental analysis

2.2 Output Stage

However Z_{o1} is too high so we need a second stage to achieve a lower Z_o . Due to the big difference between the Z_{o1} we can be positive that no voltage signal will be lost. For the DC response of the output stage, we follow the same logic of the gain stage and we easily get $Z_{i2} = \frac{(g_{m2} + g_{\pi 2} + g_{o2} + g_{E2})}{g_{\pi 2}(g_{\pi 2} + g_{o2} + g_{E2})}$ and $Z_{o2} = \frac{1}{(g_{m2} + g_{\pi 2} + g_{o2} + g_{E2})}$. On the

other hand, to get the incremental response we have to create another model like Fig.3. Using nodal analysis we end up with $A_{v2} = \frac{v_{o2}}{v_{i2}} = \frac{g_{\pi} + g_{m2}}{g_{\pi2} + g_{z2} + g_{o2} + g_{m2}}$ for the gain.

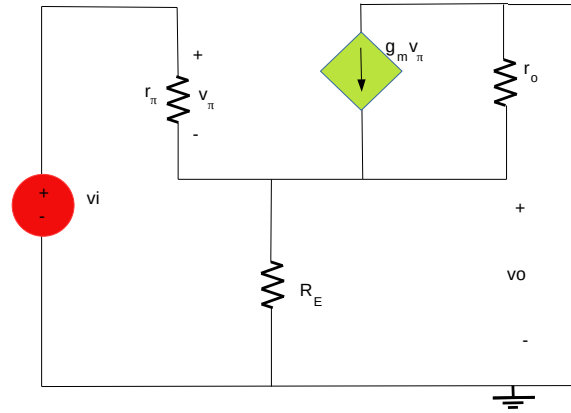


Figure 3: Model for the output stage incremental analysis

2.3 Final Results

Finally, we calculated i_o to then compute $Z_o = \frac{v_o}{i_o} = \frac{1}{g_{o2} + g_{m2} \frac{r_{\pi2}}{r_{\pi2} + Z_{o1}} + g_{e2} + \frac{1}{r_{\pi2} + Z_{o1}}}$ using the provided equations.

The gain is given by $A_V = A_{V1} * A_{V2}$.

We also computed the low cutoff frequency in octave. All the important results obtained are shown in the tables and in the figure bellow. As we can see, there will not be signal loss since $Z_{i2} \gg Z_{o1}$.

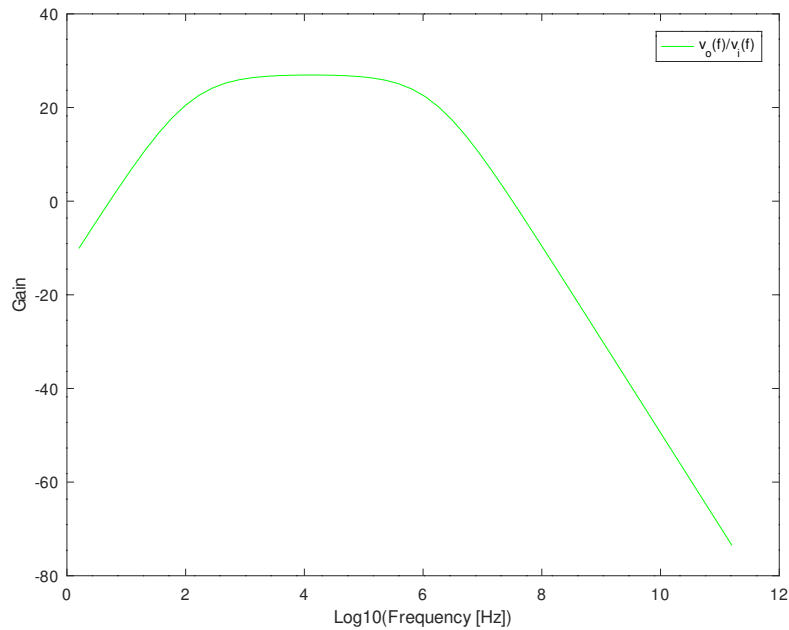


Figure 4: Voltage Gain of the circuit. Octave

Name	Value
IB1	1.975467e-05
IC1	3.530160e-03
IE1	3.549915e-03
VColl	1.409519e+00
VBase	1.090909e+00
VEmit	3.549915e-01
VCE	1.054527e+00 V
VBEON	7.000000e-01 V
VEC	2.109519e+00 V
VEBON	7.000000e-01 V
IB2	-4.332230e-04 A
IC2	9.847159e-02 A
IE2	9.890481e-02 A

Table 2: Operating point currents and Vcoll.

Name	Value
Zin1	1.640721e+03 Ohm
Zoutut1	2.604294e+03 Ohm
Zin2	7.640438e+03 Ohm
Zoutut2	2.519628e-01 Ohm
Zout	1.016161e+01

Table 3: Impedences of both stages and of the full circuit.

Name	Value
Total Gain (dB)	2.709785e+01 V
Low Cut Off Frequency	1.135794e+02 Hz
High Cut Off Frequency	1.487259e+06 Hz
Bandwidth	1.487146e+06 Hz
Cost	1.225400e+03 MU's
Merit	2.895416e+02

Table 4: Gain, bandwidth and cutoff frequency.

3 Simulation Analysis

In this section, the several steps taken using ngspice in order to conduct the simulation of the audio amplifier, as requested, will be described. The main focus of the simulation was to determine and optimize the values of the gain, the cut off frequencies, both lower and upper and the bandwidth. The quality and overall figure of merit will then be analysed. The group proceeded as follows:

1. Design of the circuit, having as a starting point the circuit given by the professor.
2. Verification of the operation of the transistors in the forward Active region, the called F.A.R mode. The results are shown below.

Vce	1.57786
Vbe	0.682323
Vce greater than Vbe	Correct F.A.R

Table 5: Verification of the F.A.R mode in the NPN transistor

Vec	2.72908
Veb	0.781397
Vec greater than Veb	Correct F.A.R

Table 6: Verification of the F.A.R mode in the NPN transistor

3. OP Analysis

Then, the OP values of the currents and nodal voltages were computed. These are key to calculate the incremental parameters. The results are compared to the Ocatve results in section 4.

4. In the frequency domain, measure of the output voltage gain, using the function .meas as well as the lower and upper cut off frequencies and the bandwidth.

V Gain	36.3869
Bandwidth	1.27868E+06
Lower Cut Off Freq	53.0031

Table 7: Results for ngspice

The quantities obtained are described in the table 7. The results obtained allowed the group to understand the functions of the different components of the circuit. The conclusions will be outlined.

EFFECT OF THE COUPLING CAPACITORS

The coupling capacitors' main porpuse is to block the DC signals. If studying an incremental model of an audio amplifier, all values that are constant must be eliminated so the transistors are always fowardly conducting. As so, two coupling capacitors were used. Once the capacitors may also block some low frequencies, they have a direct influence in the bandwidth.

EFFECT OF THE BYPASS CAPACITOR


As studied in the lectures, the resistor R_e has the funciton of stabelizing the effect of the temperature in the DC voltage. However, it has also a negative effect on the gain, once it lowers it. In order to solve the problem, a bypass capacitor C_e is placed in parallel with the resistor, so that the capacitor bypasses the resistor. In DC mode, the resistor plays its effect in the temperature. In AC, the resistor will not affect the gain. To sum up, the capacitor is a short-circuit for higher frequencies (AC) and a open-circuit for low frequencies (DC).

EFFECT OF RC


IC is the most important current in the circuit because it determines g_m , and so directly influences the gain, by increasing it.

GRAPHICAL REPRESENTATION

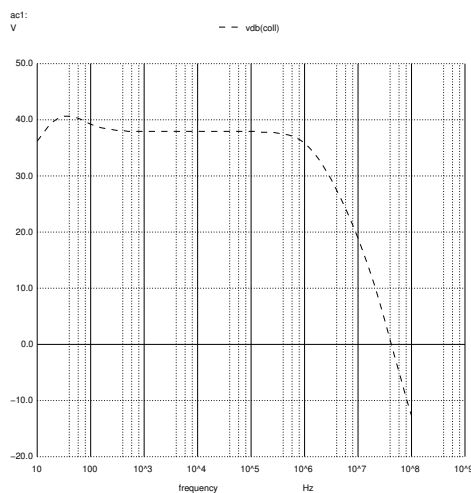In the graphics 5a and 5b, a graphic representation of the effect of the components above mentioned can be observed. In fact, in the plot 5b is extremely enlightening as one can intuitively notice the high bandwidth, the stabilization of the gain, and the gain itself.



(a) Input Voltage

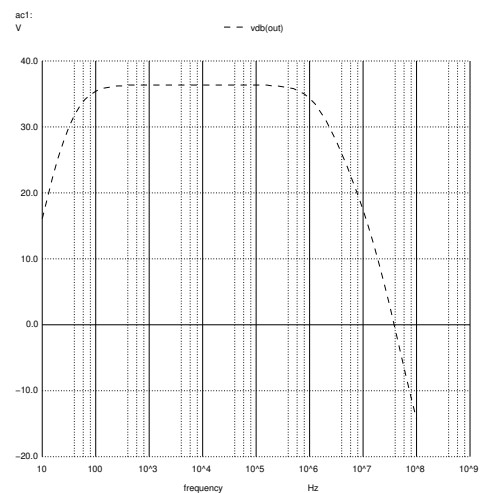

(b) Output voltage

5. Determination of the input impedance, seen from the input voltage source.

Zin	$-738.418 + 125.718 j$
-----	------------------------

Table 8: Input impedance in Ohm

The result obtained for the input impedance, considering the value in Ohm, is high. This is beneficial for the gain, because the voltage in the node In 2 must be as similar to V_{in} as possible. Using a voltage divider, the only way to achieve this was to have a very high resistance value.

6. Determination of the output impedance, using a different set up, seen from the load resistance.

Zo	$22.5223 + 0.359649 j$
Zo(arg)	22.5252

Table 9: Output impedance in Ohm

Concerning the output impedance, an opposite deduction to the one made for the output impedance is mandatory. Considering a voltage divider, the output impedance must be as low as possible, in order to the output voltage to be as high as possible. Having said that, an analysing tables 8 9, the difference needed between the two is confirmed. The output impedance obtained is favorable to the 8 Ohm load resistance.

7. Compute of the cost and figure of merit

To finally understand the efficiency of the amplifier, the cost and figure of merit were calculated

Cost	1225.6
merit	716.238

Table 10: Cost and Figure of merit

Analysing table 10, the results obtained may be considered satisfying.

4 Comparison

In this section, a global comparison between Octave and Ngspice results will be made. Firstly, one should bear in mind that, in the previous sections, an Operating Point Analysis was performed to find the necessary values for the Incremental Analysis. Therefore, in the table below, the voltages in the collector, base and emitter of the transistor are presented as well as the currents in each terminal (I_B , I_C , I_E).

Calculus	Value [A or V]
@cb[i]	0.000000e+00
@ci[i]	0.000000e+00
@cout[i]	0.000000e+00
@q1[ib]	2.132105e-05
@q1[ic]	3.676881e-03
@q1[ie]	-3.69820e-03
@q1[is]	1.945288e-12
@q2[ib]	3.261073e-04
@q2[ic]	4.602851e-02
@q2[ie]	-4.63546e-02
@q2[is]	-1.94801e-12
@r1[i]	5.473928e-04
@r2[i]	5.260718e-04
@rc[i]	3.350773e-03
@re[i]	3.698202e-03
@rin[i]	0.000000e+00
@rl[i]	0.000000e+00
@rout[i]	-4.63546e-02
base	1.052144e+00
coll	1.947680e+00
emit	3.698202e-01
emit2	2.729077e+00
in	0.000000e+00
in2	0.000000e+00
out	0.000000e+00
vbe	6.823234e-01
vcc	1.200000e+01
vce	1.577860e+00
veb	7.813967e-01
vec	2.729077e+00

Name	Value [A or V]
IB1	1.975467e-05
IC1	3.530160e-03
IE1	3.549915e-03
VColl	1.409519e+00
VBase	1.090909e+00
VEmit	3.549915e-01
VCE	1.054527e+00 V
VBEON	7.000000e-01 V
VEC	2.109519e+00 V
VEBON	7.000000e-01 V
IB2	-4.332230e-04 A
IC2	9.847159e-02 A
IE2	9.890481e-02 A

Table 12: Operating point using DC model. Variables are expressed in Ampere or Volt.(Octave)

Table 11: Operating point using DC model. Variables are expressed in Ampere or Volt. (Ngspice)

As one may observe, some discrepancies in the voltage values are noticeable. Nevertheless, the values of the currents flowing are within reasonable intervals of similarity. Therefore, the gain computed in Octave should not be severely affected by this. It is important to highlight that the theoretical gain expression is dependent on the value of the current I_C because of the incremental parameter g_m .

Calculus	Value
V Gain	36.3869
Low Cut Off Freq	53.0031
High Cut Off Freq	1.27873E+06
Bandwidth	1.27868E+06
Cost	1225.6
merit	716.238

Name	Value
Total Gain (dB)	2.709785e+01 V
Low Cut Off Frequency	1.135794e+02 Hz
High Cut Off Frequency	1.487259e+06 Hz
Bandwidth	1.487146e+06 Hz
Cost	1.225400e+03 MU's
Merit	2.895416e+02

Table 13: Gain, bandwidth and cut off frequency. (Ngspice) Table 14: Gain, bandwidth and cut off frequency. (Octave)

Additionally, the gain, bandwidth and cut off frequency results were also computed. As predicted, the voltage gain in the theoretical approach is greater than in the Ngspice computation. Moreover, since we do not have the theoretical high cut frequency, we can only compare the results for the low cut frequency, which are very similar as far as the order of magnitude is concerned. For this reason, as the bandwidth is the subtraction between high and low cut frequencies, it should not be compared.

5 Conclusion

As discussed in the introduction, the main goal of this assignment was to project an audio amplifier that allowed maximum voltage gain, spending the less possible on the components used. As so, both theoretical analysis and simulation analyses were conducted.

Despite strong efforts to match the results obtained in the different analysis, it was concluded that, due to the non-linearity of the components of the circuit, particularly the transistors, it was impossible to obtain the exact same quality using both tools. In fact, the complexity of the parameters of the transistors used in ngspice is believed to be the main reason for this outcome.

Nevertheless, once the ngspice model is the most similiar to reality, the model used can then be validated, disparte the discrepancies already explained.